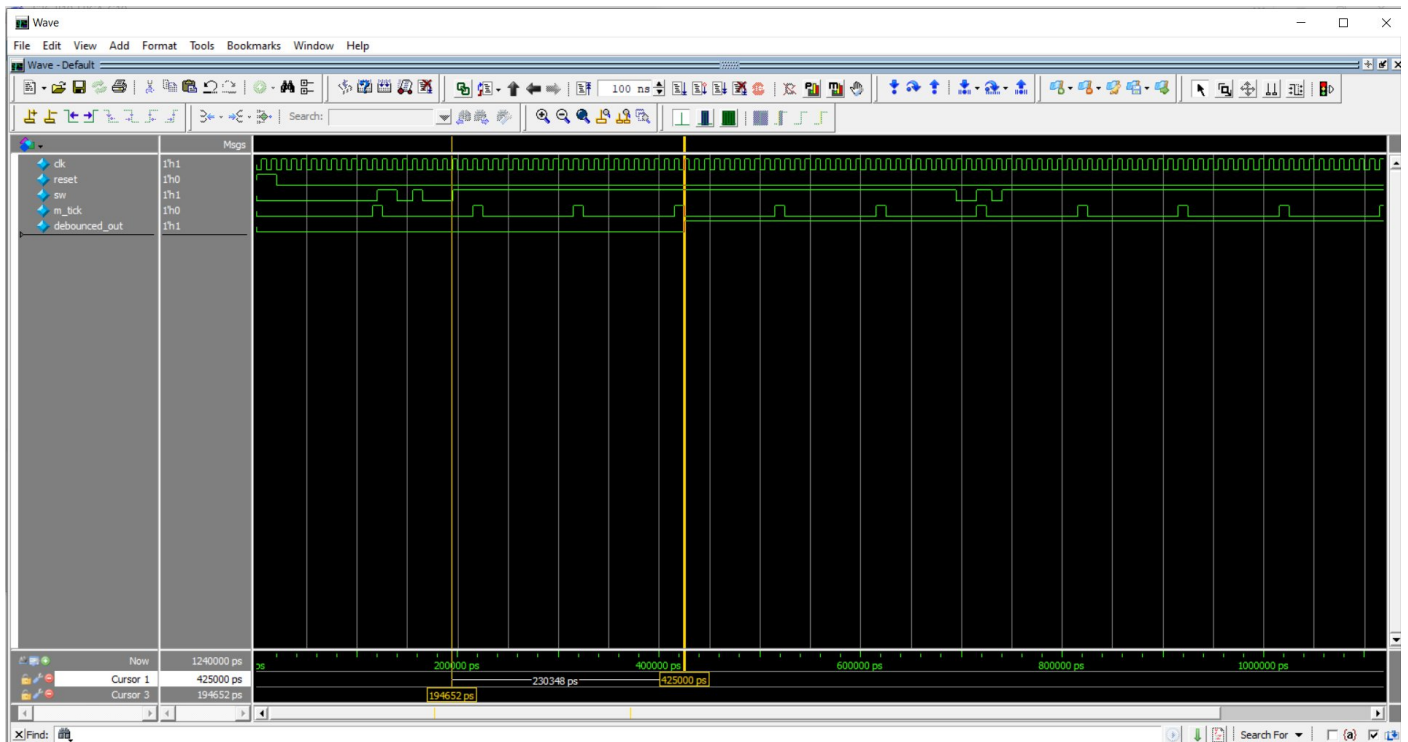


Debouncing circuit

Wave form snapshot:



Cursor 1 sits right around where `sw` has its last bounce before settling stable. Cursor 2 sits exactly where `debounced_out` makes its transition. A ~ 230 ns gap is exactly what the FSM should produce needing 3 consecutive stable `m_tick` samples before flipping the output.

This confirms the debounce delay is working as designed.