

Two_bit_full_adder

Results Summary

The gate-level, structural, and behavioral implementations of the 2-bit full adder were verified against all 32 input combinations and produced identical sum and cout outputs in every case, confirming correct carry propagation and functional equivalence across all three design styles.

Transcript		
# t=0	ala0=00 blb0=00 cin=0 gate: sumlsum0=00 cout=0 struc: sumlsum0=00 cout=0 behav: sumlsum0=00 cout=0	
# t=10	ala0=00 blb0=00 cin=1 gate: sumlsum0=01 cout=0 struc: sumlsum0=01 cout=0 behav: sumlsum0=01 cout=0	
# t=20	ala0=00 blb0=01 cin=0 gate: sumlsum0=01 cout=0 struc: sumlsum0=01 cout=0 behav: sumlsum0=01 cout=0	
# t=30	ala0=00 blb0=01 cin=1 gate: sumlsum0=10 cout=0 struc: sumlsum0=10 cout=0 behav: sumlsum0=10 cout=0	
# t=40	ala0=00 blb0=10 cin=0 gate: sumlsum0=10 cout=0 struc: sumlsum0=10 cout=0 behav: sumlsum0=10 cout=0	
# t=50	ala0=00 blb0=10 cin=1 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=60	ala0=00 blb0=11 cin=0 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=70	ala0=00 blb0=11 cin=1 gate: sumlsum0=00 cout=1 struc: sumlsum0=00 cout=1 behav: sumlsum0=00 cout=1	
# t=80	ala0=01 blb0=00 cin=0 gate: sumlsum0=01 cout=0 struc: sumlsum0=01 cout=0 behav: sumlsum0=01 cout=0	
# t=90	ala0=01 blb0=00 cin=1 gate: sumlsum0=10 cout=0 struc: sumlsum0=10 cout=0 behav: sumlsum0=10 cout=0	
# t=100	ala0=01 blb0=01 cin=0 gate: sumlsum0=10 cout=0 struc: sumlsum0=10 cout=0 behav: sumlsum0=10 cout=0	
# t=110	ala0=01 blb0=01 cin=1 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=120	ala0=01 blb0=10 cin=0 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=130	ala0=01 blb0=10 cin=1 gate: sumlsum0=00 cout=1 struc: sumlsum0=00 cout=1 behav: sumlsum0=00 cout=1	
# t=140	ala0=01 blb0=11 cin=0 gate: sumlsum0=00 cout=1 struc: sumlsum0=00 cout=1 behav: sumlsum0=00 cout=1	
# t=150	ala0=01 blb0=11 cin=1 gate: sumlsum0=01 cout=1 struc: sumlsum0=01 cout=1 behav: sumlsum0=01 cout=1	
# t=160	ala0=10 blb0=00 cin=0 gate: sumlsum0=10 cout=0 struc: sumlsum0=10 cout=0 behav: sumlsum0=10 cout=0	
# t=170	ala0=10 blb0=00 cin=1 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=180	ala0=10 blb0=01 cin=0 gate: sumlsum0=11 cout=0 struc: sumlsum0=11 cout=0 behav: sumlsum0=11 cout=0	
# t=190	ala0=10 blb0=01 cin=1 gate: sumlsum0=00 cout=1 struc: sumlsum0=00 cout=1 behav: sumlsum0=00 cout=1	
# t=200	ala0=10 blb0=10 cin=0 gate: sumlsum0=00 cout=1 struc: sumlsum0=00 cout=1 behav: sumlsum0=00 cout=1	
Project : fa Now: 320 ns Delta: 0 sim:/two_bit_full_adder_tb/#INITIAL#37		

